

Computer Mathematics

Week 8

Combinational logic circuits

the mathematics of logic circuits

- the foundation of all digital design

Boolean logic


- when 0 and 1 represent true and false

Boolean algebra

- Boolean functions
- canonical forms

simplification of Boolean expressions

- de Morgan's laws

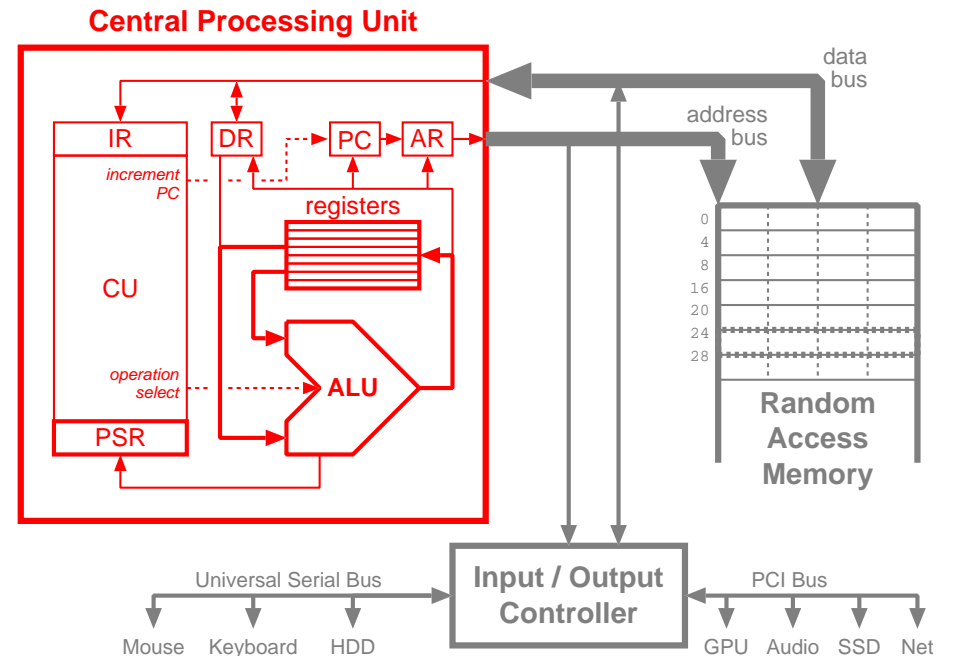

combinational digital circuits


wires, signals and connections

logic gates

- and, or, not
- nand, nor, xor

gate-level arithmetic operations


- how logic turns into addition

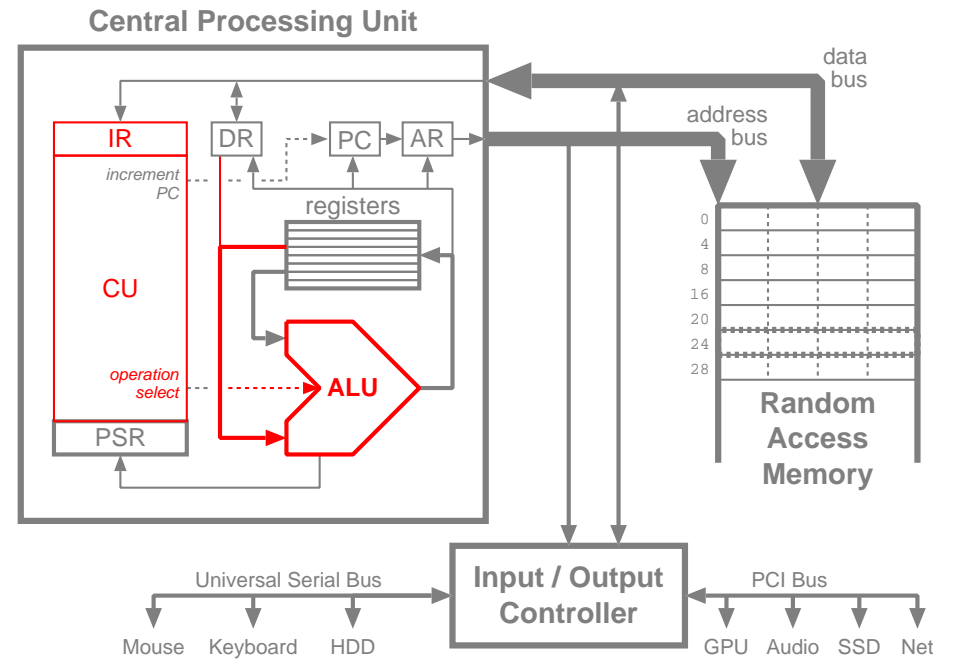

logic gates

logic *gates* implement Boolean operations

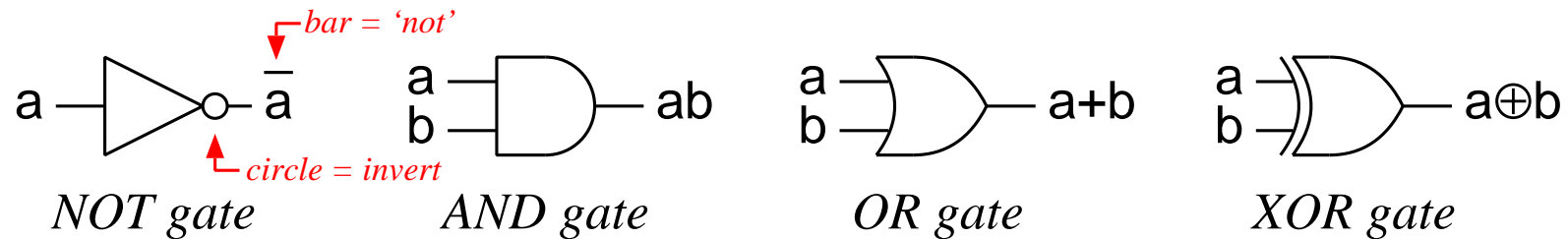- one or more inputs, one or more outputs
- outputs are a logical function of the inputs
- logic circuits use electrical engineering notation, not mathematical notation



another useful gate: *exclusive-or* (XOR)

- not equivalent, or modulo-2 addition/subtraction
- very useful for arithmetic operations

a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0


beware: $\overline{ab} = (a \cdot b)'$, but $\bar{a}\bar{b} = a' \cdot b' = (a + b)'$

- use an explicit '.' if it helps readability, e.g., $\bar{a} \cdot \bar{b}$


more logic gates

the small circle indicates an inversion

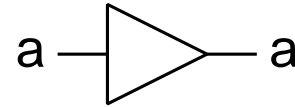- an *active-low* signal ('not' function)
- written with an overbar




buffer (no change)

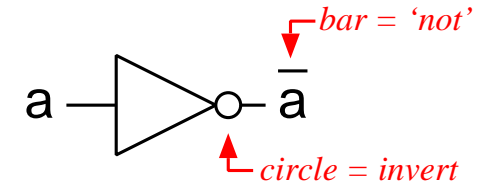


NOT gate (inverter)

it can be placed on any output (or input)

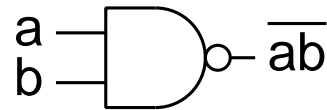
- when 'true' that output (or input) will be 0
- NAND = 'not AND', NOR = 'not OR', XNOR = 'not XOR'



NAND gate

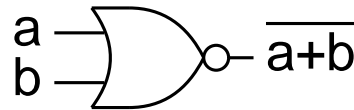

NOR gate

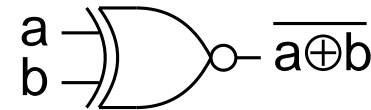

XNOR gate

NAND		
<i>a</i>	<i>b</i>	\overline{ab}
0	0	1
0	1	1
1	0	1
1	1	0

NOR		
<i>a</i>	<i>b</i>	$\overline{a+b}$
0	0	1
0	1	0
1	0	0
1	1	0

XNOR		
<i>a</i>	<i>b</i>	$\overline{a \oplus b}$
0	0	1
0	1	0
1	0	0
1	1	1

wires, signals, and connections

signals


- a *signal* is anything that conveys a logic value (or other message)

wires

- a *wire* carries a signal between two or more points in an electrical circuit
- all points connected by the wire have the same logic value



named signals

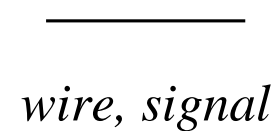- any signal can be given a name
- circuit inputs and outputs are usually named
- intermediate signals can be named, to show logical relationships



connections

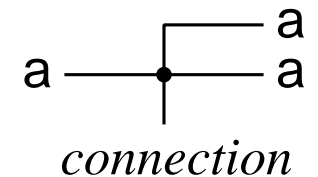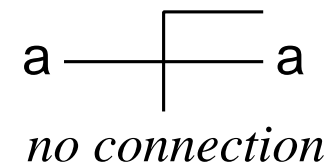- crossing wires have no connection
- unless an explicit connecting dot is present




Boolean logic and functions

- logical operators perform computation
- operands transmit values implicitly (results of \cdot to input of $+$ below)
- variables transmit values explicitly (e.g., function parameters to expression)

$$\text{equal}(a, b) = a \cdot b + a' \cdot b'$$

logic circuits

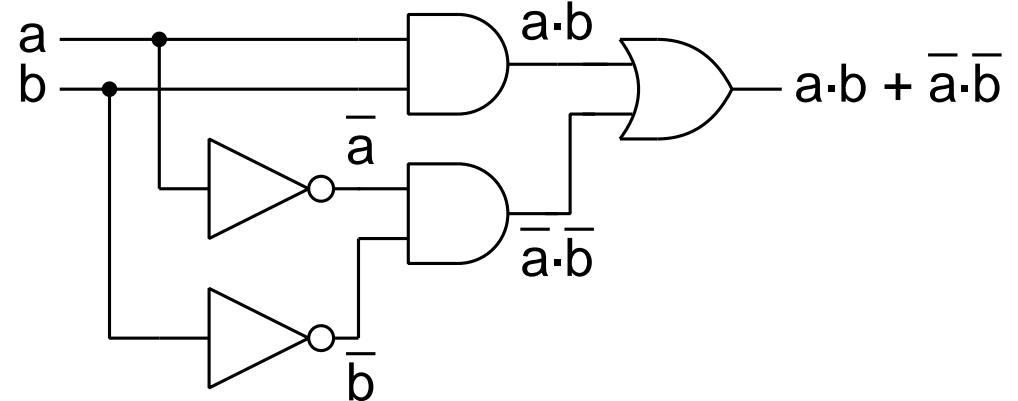- logic gates perform computation
- wires transmit values explicitly
- signal names can transmit values implicitly
(a and b could be generated elsewhere in the circuit above)
- signals typically flow left-to-right (with frequent exceptions)



abstraction — functional blocks

Boolean logic and functions

- functions provide abstraction


$$\text{equal}(a, b) = ab + a'b'$$

$$\text{any-two}(a, b, c) = \text{equal}(a, b) + \text{equal}(a, c) + \text{equal}(b, c)$$

$$e = \text{any-two}(x, y, z)$$

logic circuits

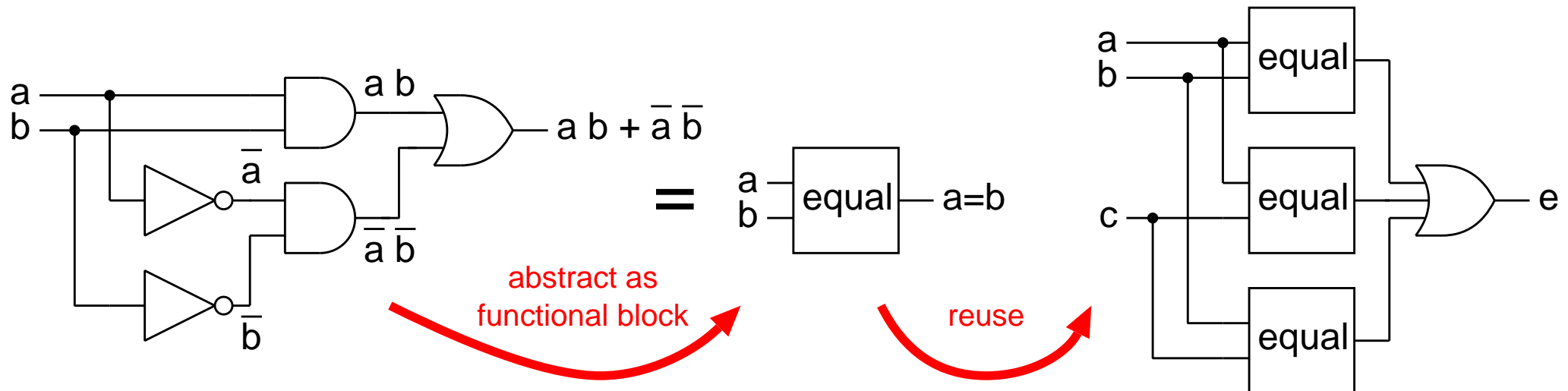- functional blocks* (components) provide abstraction



Boolean function to logic circuit

e.g., single-bit addition of two inputs

- sum is 1 if exactly one of a and b is 1 (i.e., $a \neq b \Leftrightarrow a \oplus b$)
- carry is 1 if a and b are both 1 (i.e., $a \cdot b$)


canonical form of each output

$$s = ab' + a'b = a \oplus b$$

$$c_o = ab$$

		<i>sum</i>	
<i>a</i>	<i>b</i>	c_o	<i>s</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

translated into gates

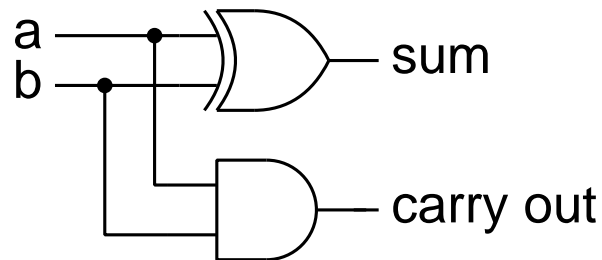

this is a *half adder*

- no provision for carry in
- not useful for multi-bit additions

addition (single-bit)

single-bit addition of three inputs

- sum is 1 if an odd number of inputs are 1
- carry is 1 if two or more inputs are 1

			<i>sum</i>	
c_i	a	b	c_o	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

canonical form of each output, simplified, translated into gates

$$s = c'_i ab' + c'_i a'b + c_i a'b' + c_i ab$$

$$= c'_i (ab' + a'b) + c_i (a'b' + ab)$$



$$= c'_i (a \oplus b) + c_i (a \oplus b)'$$

$$= c_i \oplus a \oplus b$$

$$c_o = c'_i ab + c_i a'b + c_i ab' + c_i ab$$

$$= (c'_i + c_i) ab + c_i (a'b + ab')$$

$$= ab + c_i (a \oplus b)$$

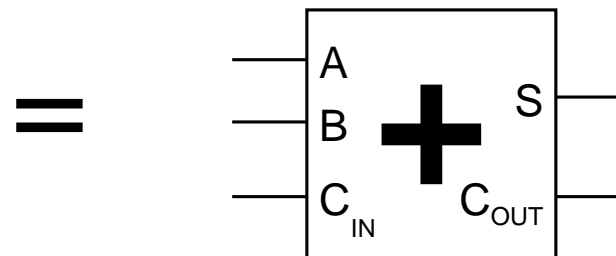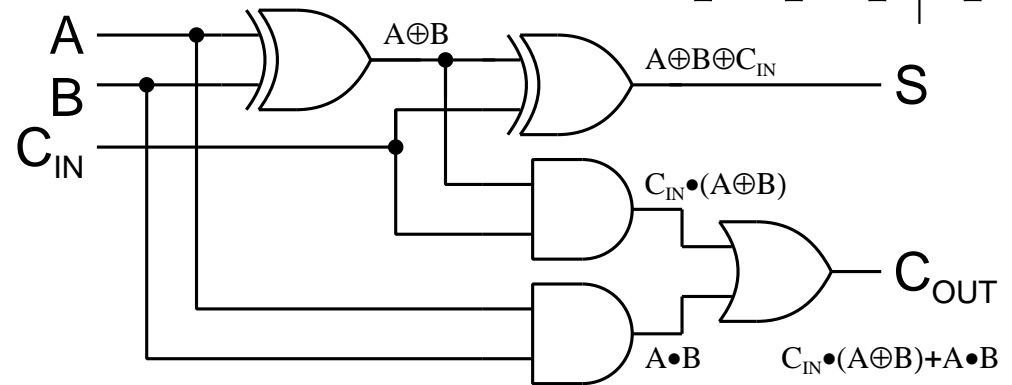

this is a *full adder*

practice drawing logic circuits for Boolean functions

consider some of the gates we did not study in detail

- how many of the logic circuits of this week can you make
 - using only NAND gates?
 - using only NOR gates?

reinforce your understanding

- write a Python program to simulate a multi-bit adder
 - consider the logical operations affecting each signal
 - compute the output of each gate based on its input(s)
 - propagate outputs to inputs at every simulation time step

ask about anything you do not understand

- from any of the classes so far this semester (or the lecture notes)
- it will be too late for you to try to catch up later!
- I am always happy to explain things differently and practice examples with you

signals and busses

gate-level multi-bit logical operations


- bitwise: and, or, not

gate-level multi-bit arithmetic operations

- addition, subtraction (unsigned, 2's complement)

1-of- N selection

- multiplexers

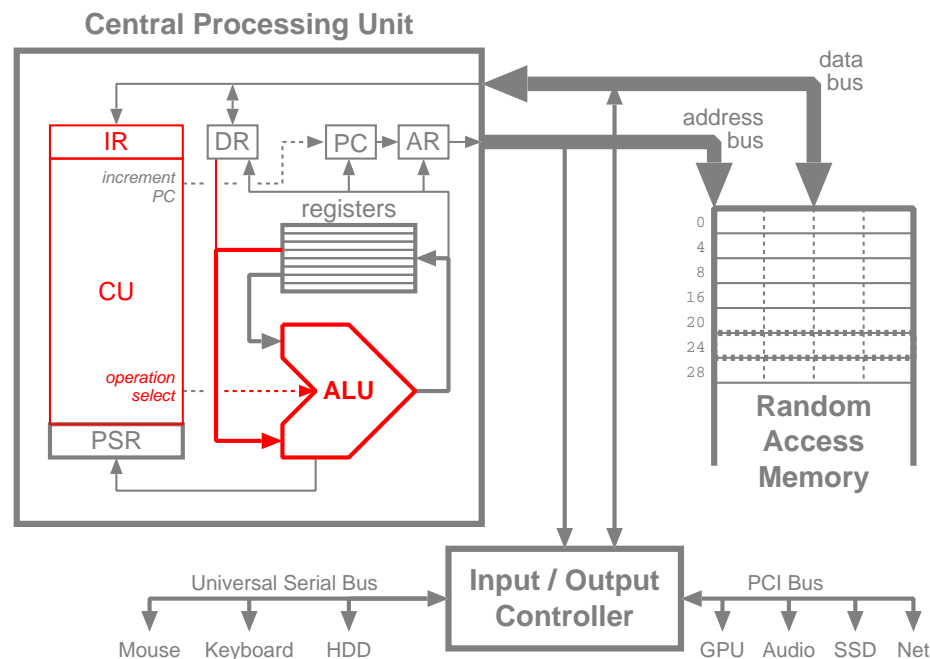

glossary

active-low — a signal that is considered ‘true’ when 0.

active-high — a signal that is considered ‘true’ when 1.

adder — a logic circuit that implements 2’s complement addition between two words of data.

carry — a processor status bit indicating that the last arithmetic operation generated an unsigned overflow (a carry out of the MS bit).

exclusive-or — an ‘or’ operation that does not allow both inputs to be the same value.

full adder — an adder that takes three single-bit inputs (two digits and a carry in) and produces two single-bit outputs (a sum and a carry out).

functional block — a high-level abstract component in a digital circuit that represents a reusable pattern of lower-level components or gates.

gate — an logic circuit component that implements a fundamental Boolean operation.

half adder — an adder that takes two single-digit inputs and produces a sum and carry output.

signal — anything that conveys a logic value from one place to another. In logic circuits, a signal is carried by a wire.

wire — a connection between several points in a circuit that forces them to all have the same logical value.