

# Computer Mathematics

Week 9

Parallel logic circuits

the mathematics of logic circuits

- the foundation of all digital design

Boolean logic


- when 0 and 1 represent true and false

Boolean algebra

- Boolean functions
- canonical forms

simplification of Boolean expressions

- de Morgan's laws

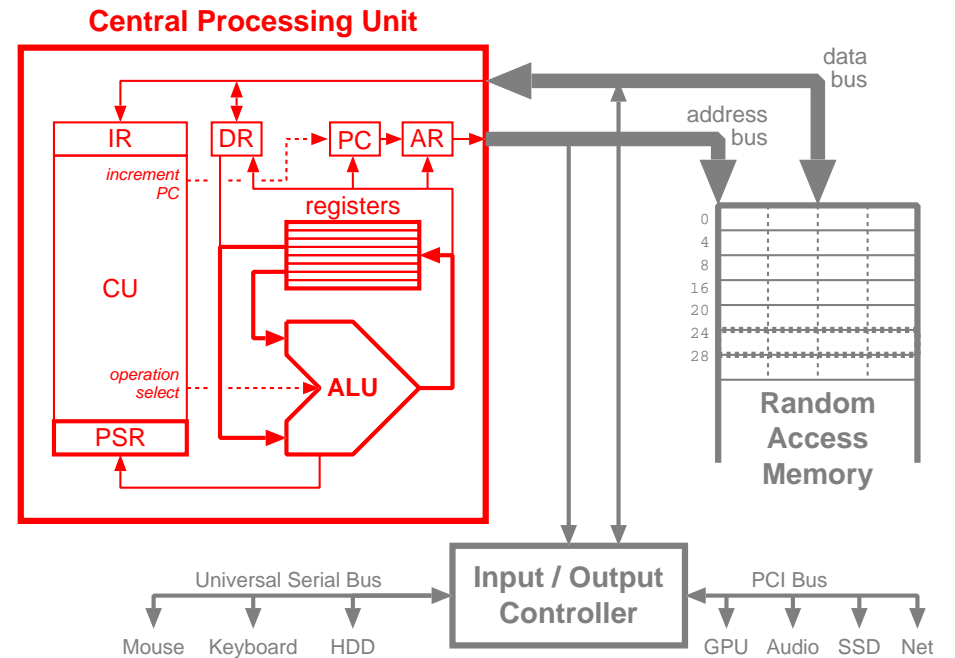

combinational digital circuits

signals and busses

logic gates

- and, or, not
- nand, nor, xor

gate-level multi-bit logical operations


- bitwise: and, or, not

gate-level multi-bit arithmetic operations

- addition, subtraction (unsigned, 2's complement)

1-of- $N$  selection

- multiplexers

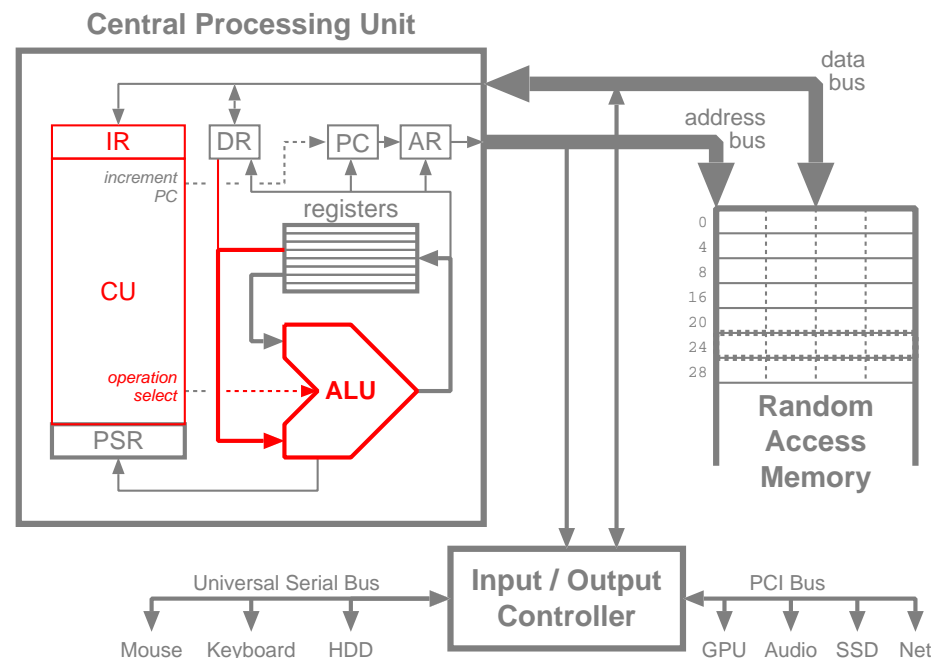

# review: addition (single-bit)

single-bit addition of three inputs

- sum is 1 if an odd number of inputs are 1
- carry is 1 if two or more inputs are 1

canonical form of each output, simplified, translated into gates

inputs			sum	
$c_i$	$a$	$b$	$c_o$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s = c'_i ab' + c'_i a'b + c_i a'b' + c_i ab$$

$$= c'_i (ab' + a'b) + c_i (a'b' + ab)$$



$$= c'_i (a \oplus b) + c_i (a \oplus b)'$$

$$= c_i \oplus a \oplus b$$

$$c_o = c'_i ab + c_i a'b + c_i ab' + c_i ab$$

$$= (c'_i + c_i) ab + c_i (a'b + ab')$$


$$= ab + c_i (a \oplus b)$$

 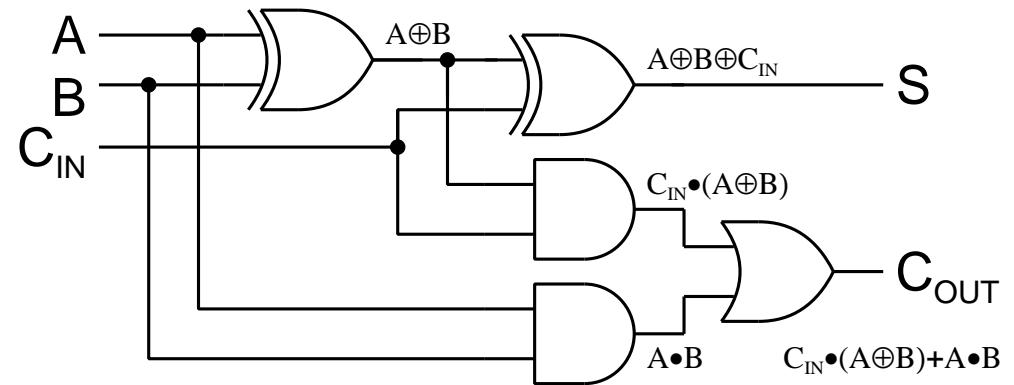


this is a *full adder*

# addition (multi-bit)

two full adders make a two-bit adder

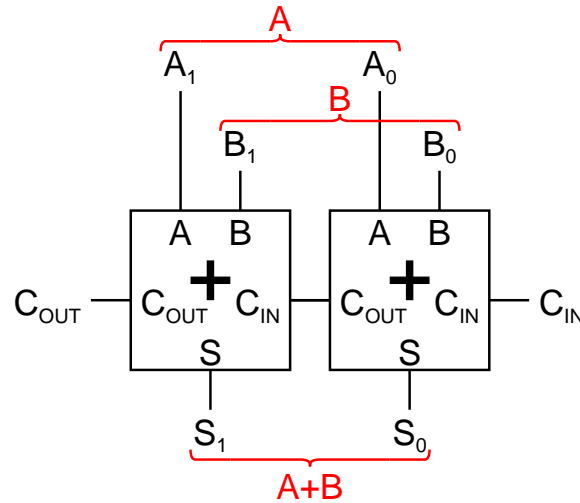

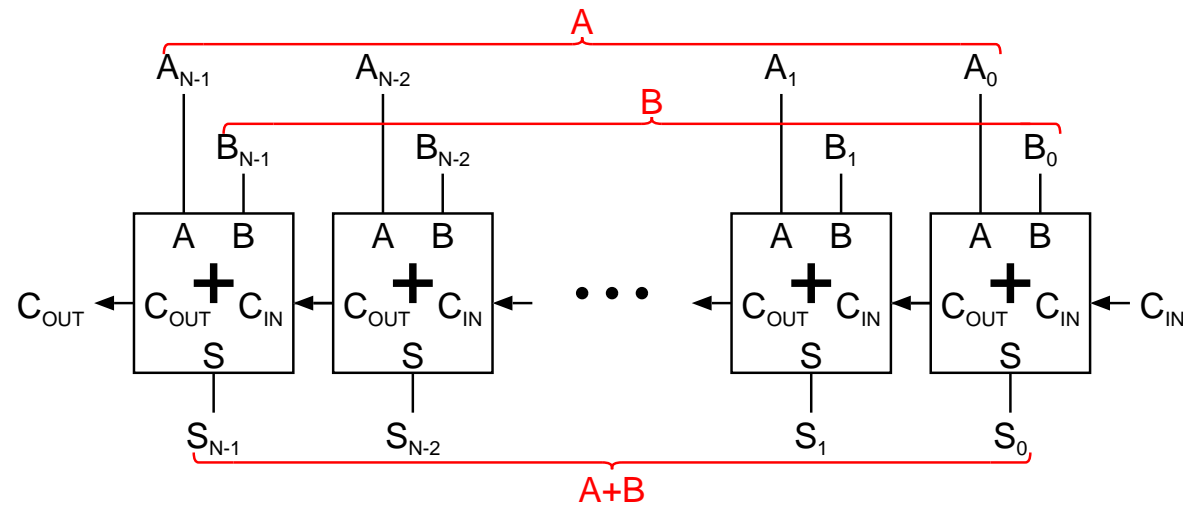to make a  $N$ -bit adder, just *daisy chain*  $N$  single-bit full adders together



(this is called a *ripple-carry adder* — is there a limit to  $N$ ?)


# abstraction — busses

writing the  $N$  separate wires (and adders) for each bit is tedious

- all  $N$  wires carrying  $A_i$  spend most of their time going to the same places
- similarly for  $B$  and  $S$


a *bus* carries many individuals in parallel between two points

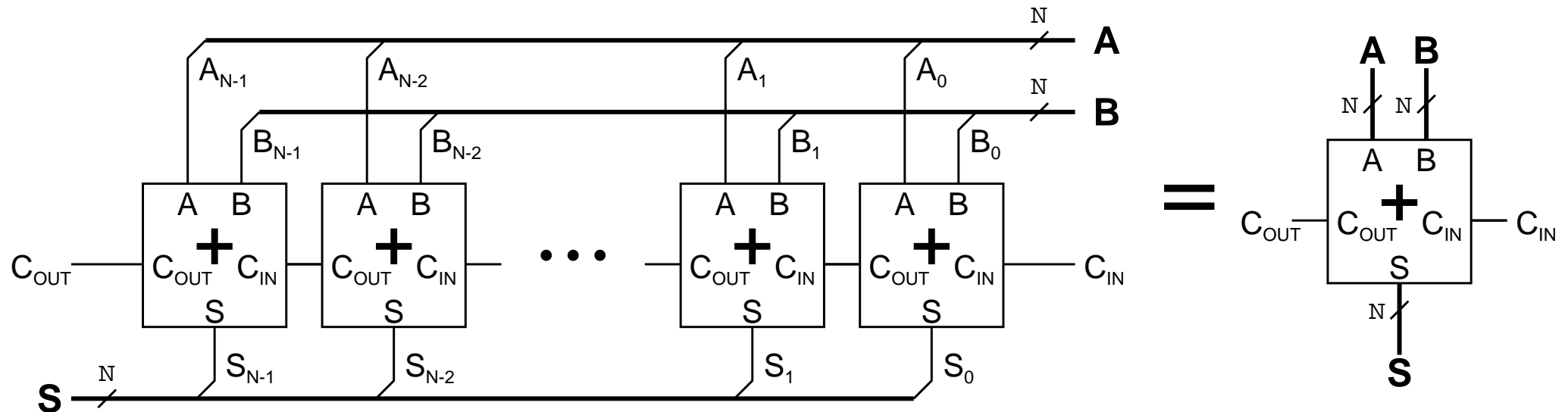- collect all the  $A_i$  together and put them on a single bus called  $A$
- similarly for  $B$  and  $S$



# busses


busses are thicker than wires

 

busses make wide turns




 wires joining or leaving a bus do so at an angle



connecting two busses sometimes uses strange symbols to indicate what is happening

- we will just draw a dot, as with wires

 

# bitwise (multi-bit) logic operations

bitwise logical operations apply a logical operation in parallel to all the bits in a word

e.g., whereas 'not' inverts a single logical value

- $0 \rightarrow 1$  and  $1 \rightarrow 0$

bitwise 'not' inverts all the bits in a word

- it is the 'one's *complement*' operation

$$\begin{array}{r} \sim 01101001 \\ \hline 10010110 \end{array}$$

similarly for AND, OR, and XOR


- AND clears (or selects) bits
- OR sets bits
- XOR inverts bits

	AND	OR	XOR
	11110000	11110000	11110000
&	<u>00110011</u>	<u>00110011</u>	⊕ <u>00110011</u>
	00110000	11110011	11000011


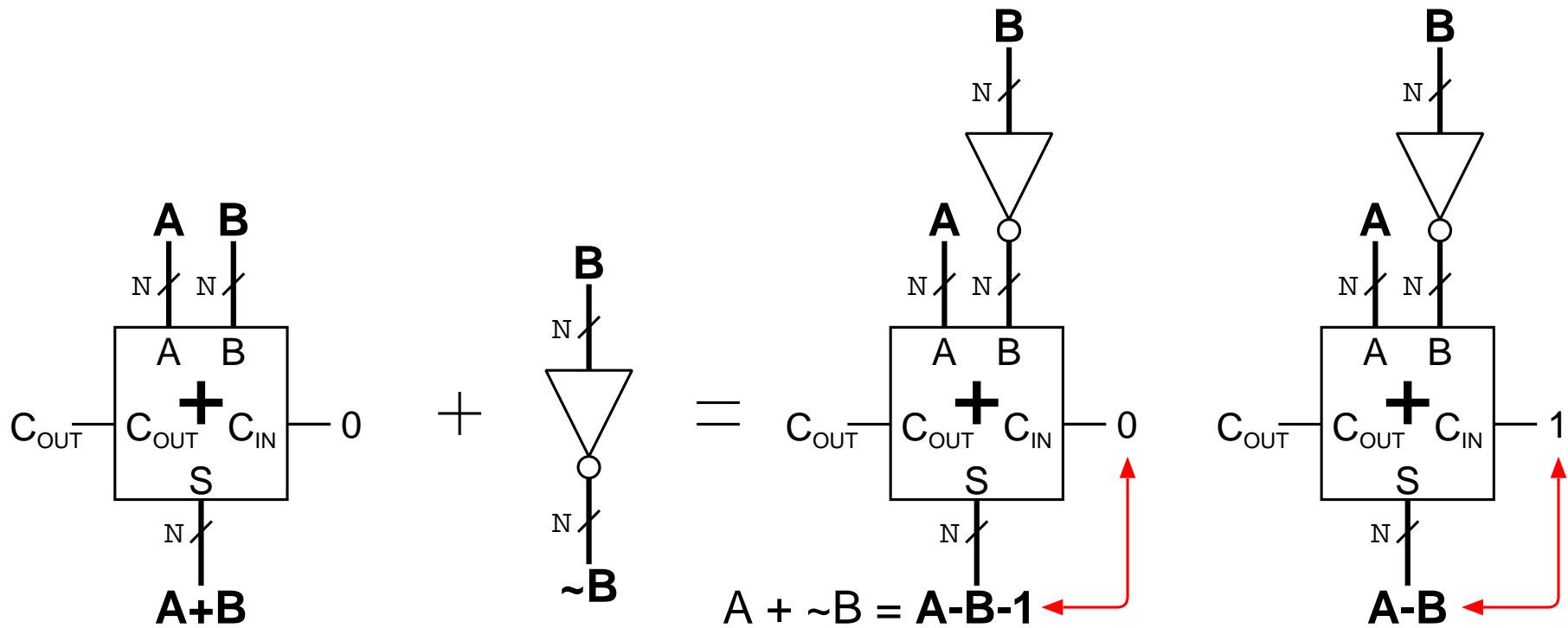
# subtraction

combine an adder with a bitwise complement to make a *subtractor*



but for correct results, we need to add the 2's complement of  $B$


to turn a 1's complement into a 2's complement negation, just add 1

- e.g., by setting  $C_{IN} = 1$
- $C_{IN}$  = 'not borrow' when performing subtraction
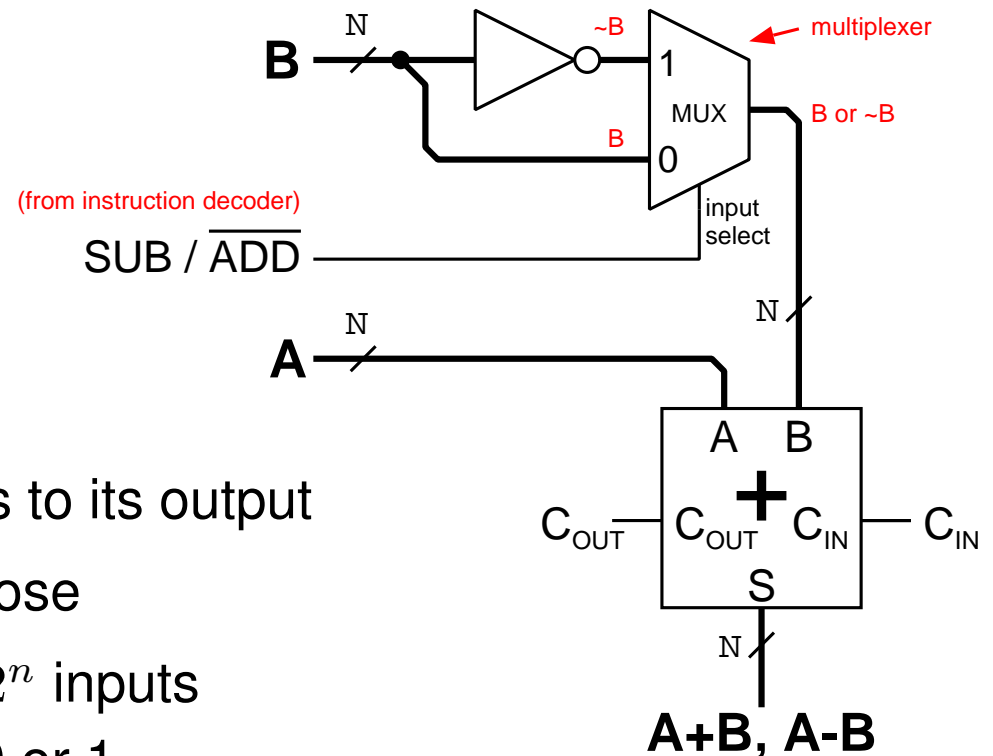
# selection

are separate adder and subtractor required?

- they are almost identical, except for the complemented  $B$  input
- if we could choose between  $B$  and  $\sim B$ , one adder would be enough



a *multiplexer* connects one of several inputs to its output

- a *select* input specifies the input to choose
- $n$ -bit select input can choose between  $2^n$  inputs
  - 1 select bit chooses between input 0 or 1
  - 2 select bits choose between inputs 0...3, etc.


# multiplexers

## 2-input multiplexer

- truth table
- Karnaugh map
- circuit
- functional block

$SEL$	$A$	$B$	$OUT$	=	$SEL$	$A$	$B$	$OUT$
0	$x$	—	$x$		0	0	0	0
1	—	$y$	$y$		0	0	1	0
					0	1	0	1
					0	1	1	1
					1	0	0	0
					1	0	1	1
					1	1	0	0
					1	1	1	1


('—' = 'don't care')

 


$$P = \overline{SEL} \cdot A$$

$$Q = SEL \cdot B$$
 
$$OUT = \overline{SEL} \cdot A + SEL \cdot B$$



# arithmetic and logic unit

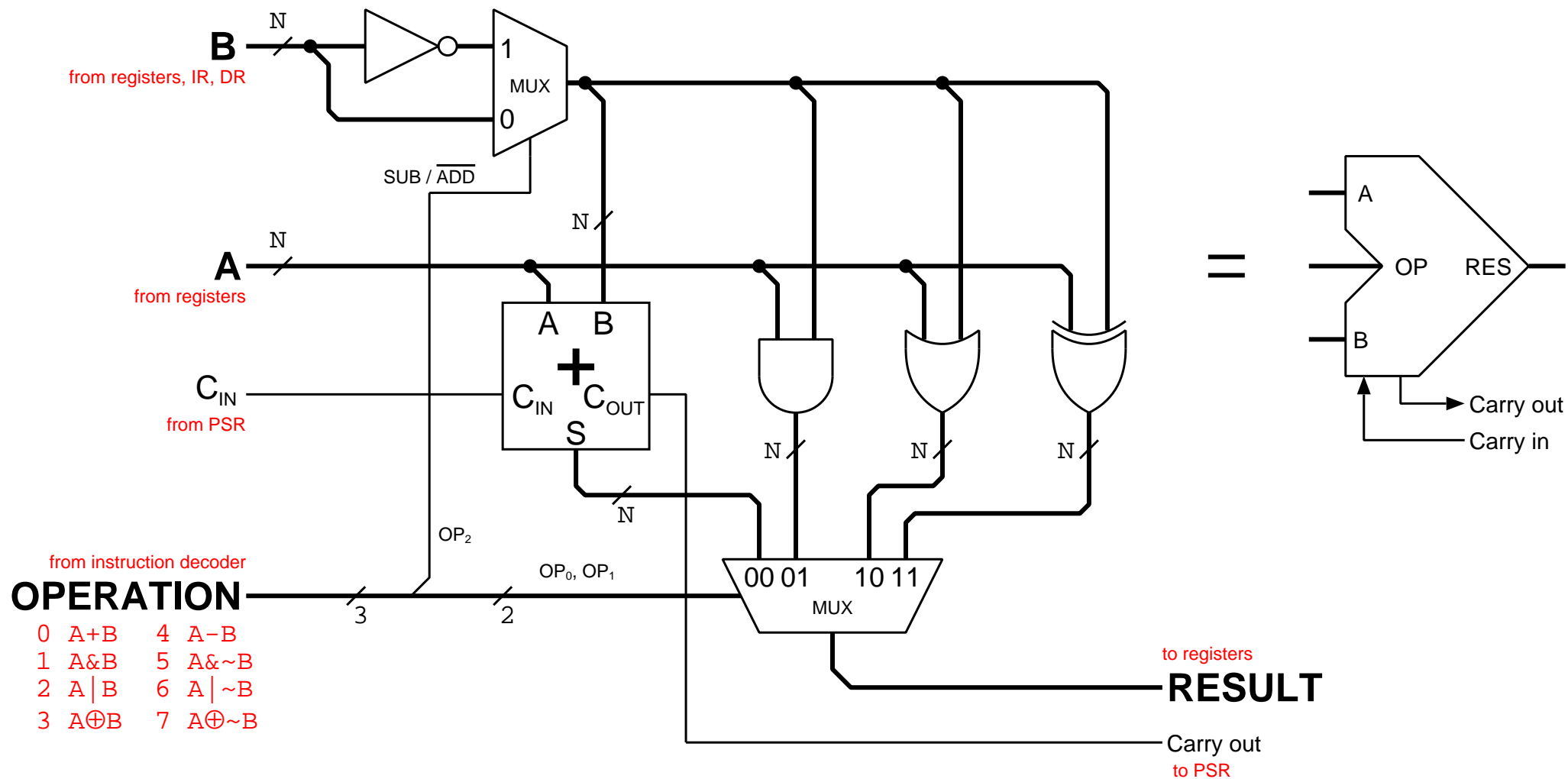

# a typical machine program

search an array to find the index of a particular value, assuming that

- the variable `array` holds the address of the start of the array
- the variable `length` holds the length of the array
- the variable `value` holds the target value that we are searching for
- the index of the element should be returned in register `r0`
- if the target is not found, `-1` should be returned in `r0`

<i>label</i>	<i>operation</i>	<i>operands</i>	<i>comment</i>
	load	r1, array	load array address into register 1
	load	r2, length	load array length into register 2
	load	r3, value	load target value into register 3
	set	r0, 0	the next index to check is held in r0
next:	compare	r0, r2	check if we reached the end of the array
	jump_if_equal	fail	if so, target was not found
	load	r4, r1[r0]	fetch next element from array
	compare	r4, r3	compare it to the target value
	jump_if_equal	done	if found, return the corresponding index in r0
→	<b>add</b>	<b>r0, r0, 1</b>	<b>increment the index</b>
	jump	next	continue searching at the next index
fail:	set	r0, -1	index -1 means 'target not found'
done:	halt		r0 contains index of target element, or -1

# instruction execution

machine ('fetch-execute') cycle:  
**repeat**

1. **fetch instruction**

- copy PC to address bus
- read from memory into IR

2. **decode instruction**

- CU inspects the IR

3. **fetch operand(s)**

- move data from memory into DR, if required
- present DR and/or registers to ALU

4. **execute instruction**

- ALU performs operation on data


5. **store result**

- write ALU output into register or memory

6. **update PC**

- with the address of the next instruction

**forever**

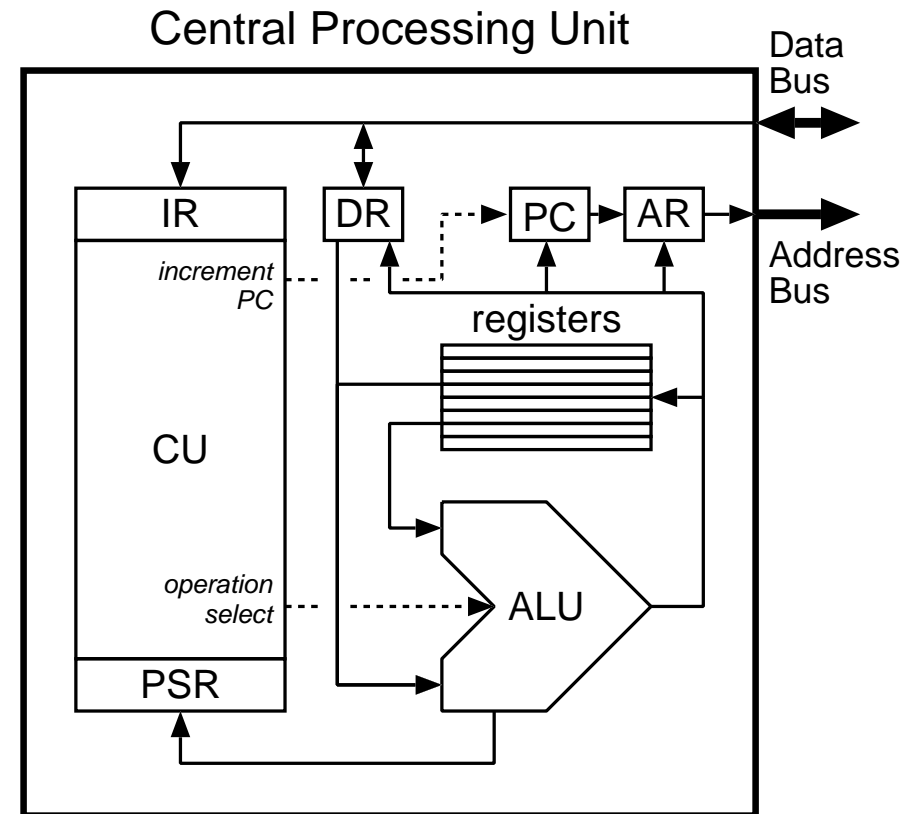


DR: data register, holds data read from memory while ALU performs an operation

AR: address register, holds address for memory read/write operation
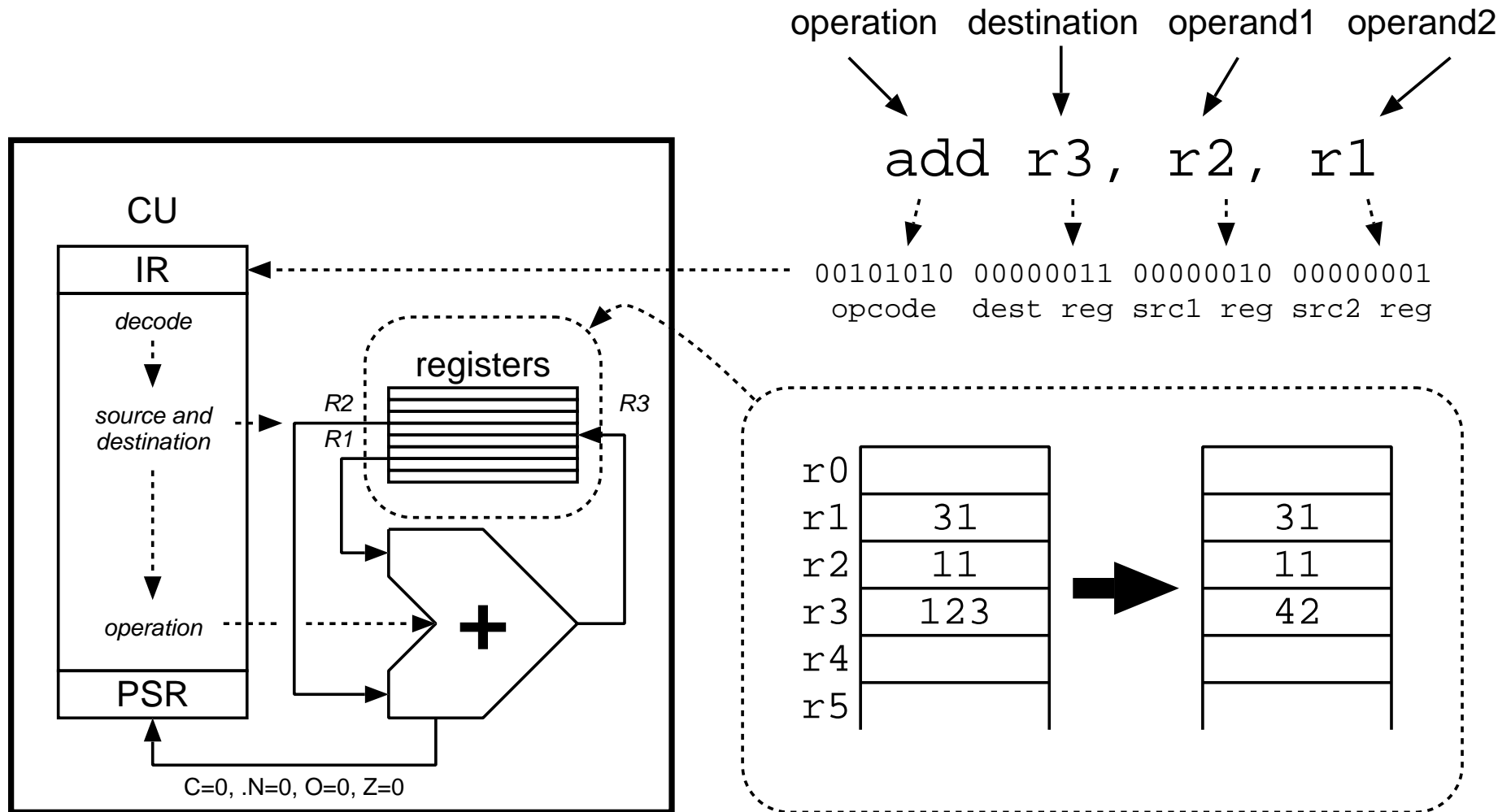
# a typical machine instruction

add register 1 to register 2, putting the result in register 3




# processor status results


also of interest: '*flags*' for updating the *processor status register*

- was the result zero, or negative?
- did unsigned or signed overflow occur?

 the result was *zero* if none of the result bits is 1




 the result was *negative* if the most-significant result bit is 1




unsigned arithmetic overflow (*carry*) occurred in the adder if

 - the carry out of the MS bit of the result was 1



signed arithmetic *overflow* occurred in the adder if

 - the carry in to the MS bit of the result  $\neq$  the carry out of it



the condition for signed overflow is maybe a little subtle?



# processor status results — signed overflow

signed arithmetic overflow occurred in the adder if

- the carry in to the MS bit of the result  $\neq$  the carry out of it

$\Rightarrow$  the sign of the result is wrong (?)

consider a signed, 8-bit, 2's complement addition:

$0xxxxxxx$     *both positive: carry out of MS bit is always 0*  
 +  $0xxxxxxx$     *if carry in is 1, the sign will change  $\Rightarrow$  overflow*

0 ← 0 ← 0  $\Rightarrow$  ok

0 ← 1 ← 1  $\Rightarrow$  overflow

$1xxxxxxx$     *both negative: carry out of MS bit is always 1*  
 +  $1xxxxxxx$     *if carry in is 0, the sign will change  $\Rightarrow$  overflow*


1 ← 1 ← 1  $\Rightarrow$  ok

1 ← 0 ← 0  $\Rightarrow$  overflow


$0xxxxxxx$     *if carry in to MS bit is 0, carry out is also 0*  
 +  $1xxxxxxx$     *if carry in to MS bit is 1, carry out is also 1*  
 0 ← 1 ← 0    *(overflow never occurs with numbers of opposite signs)*

1 ← 0 ← 1

# ALU with processor status outputs

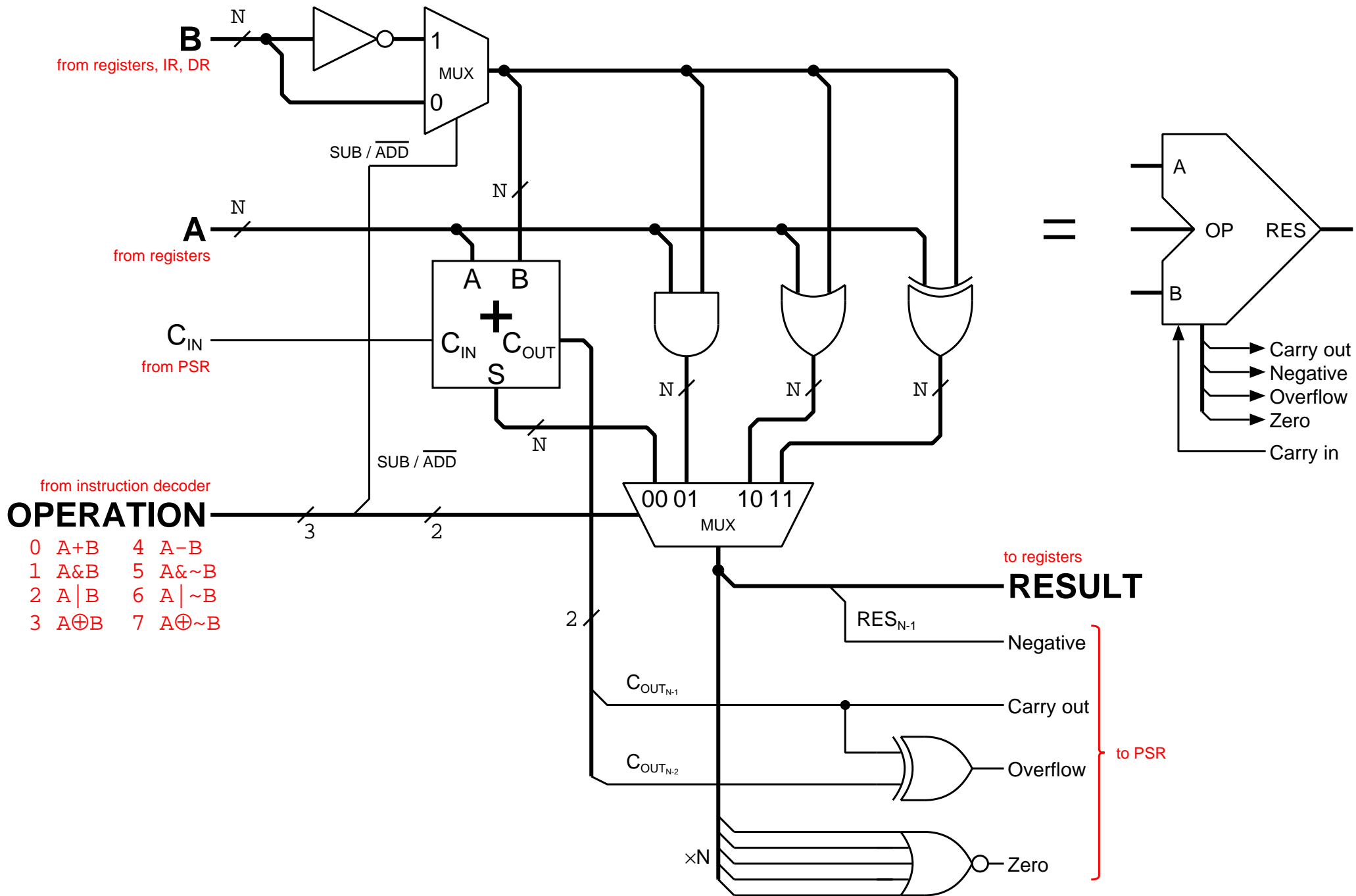
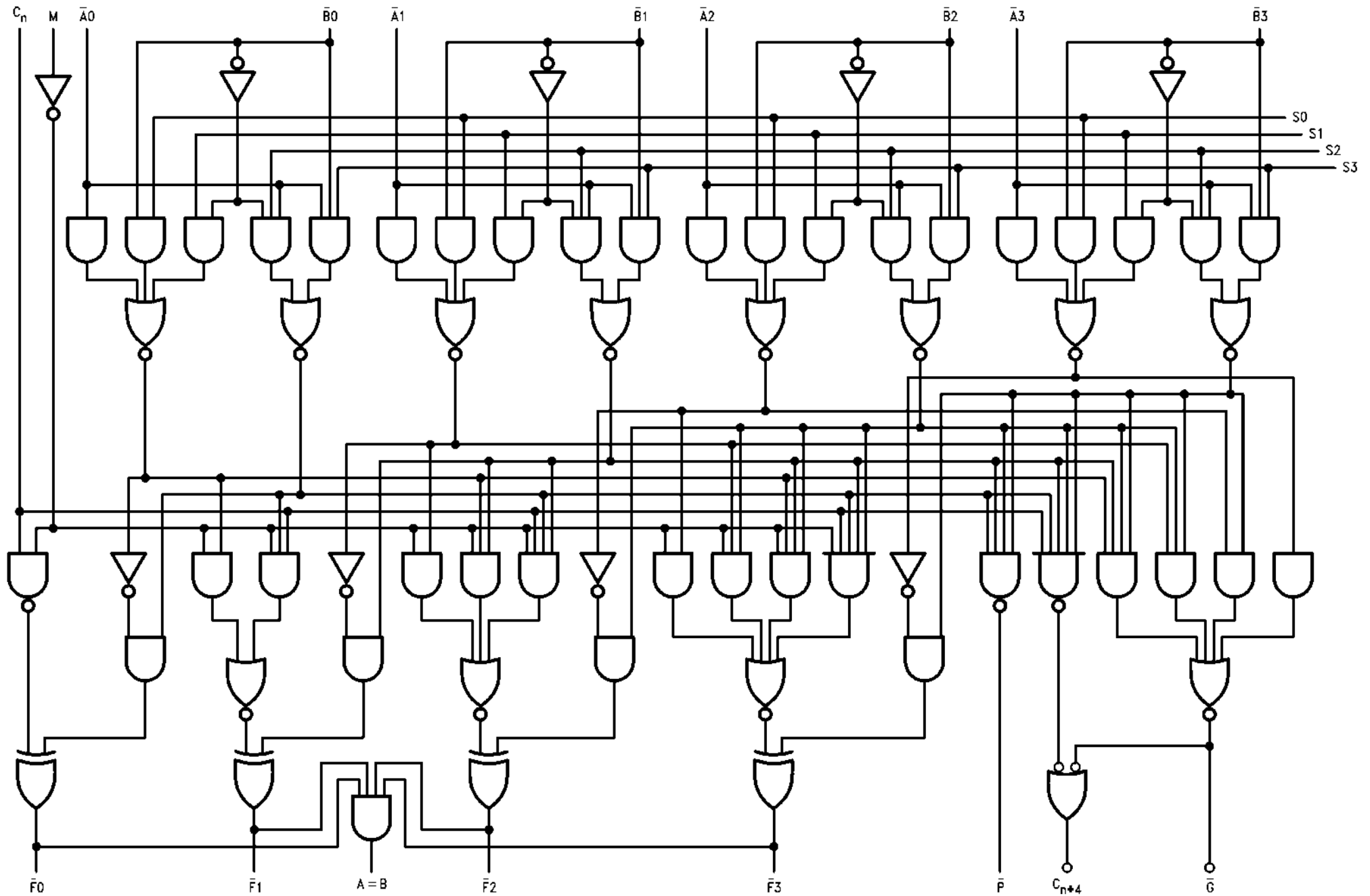
# optimised 4-bit ALU 'slice' with 32 operations



# things we did not consider

## shift and rotate instructions

- moving patterns of bits to the left or right, with or without wrap-around
- left as an exercise

## multiply instructions

- usually requires synchronous logic (next week)

## divide instructions

- always requires synchronous logic (next week)

## tri-state logic

- logic that can be 0, 1, or high-impedance
- used for bi-directional signals
- beyond the scope of this introductory course

sequential digital circuits

stateful logic

- level-triggered devices
- latches


clocks

- edge-triggered devices

synchronous logic

- flip-flops
- registers and memory

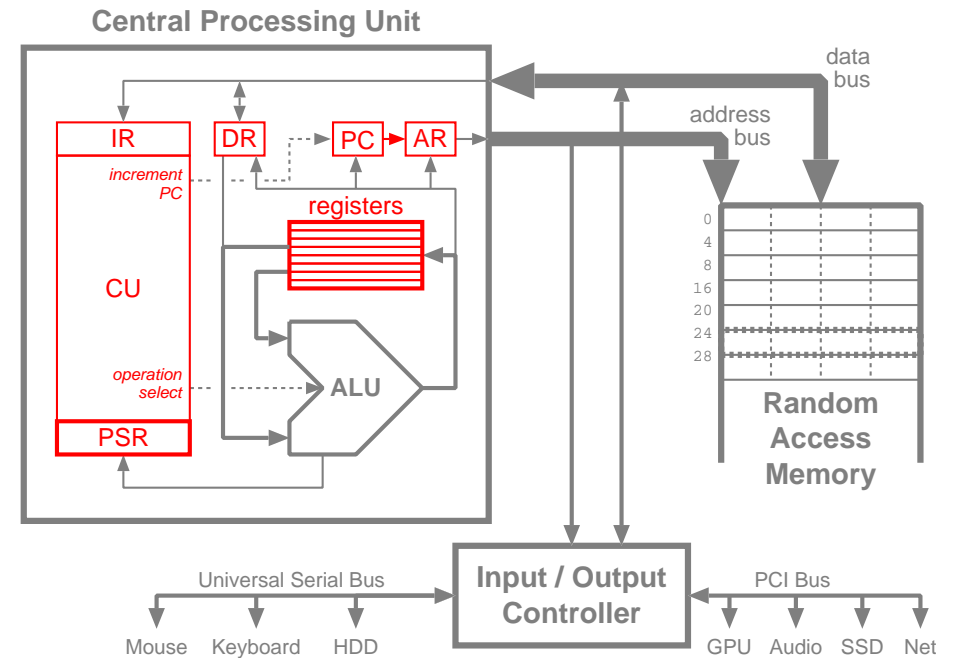CPU operation according to the clock cycle



**practice** drawing logic circuits for Boolean functions

**consider** some of the gates we did not study in detail

- how many of the logic circuits of this week can you make
  - using only NAND gates?
  - using only NOR gates?

**reinforce your understanding**

- write a Python program to simulate a multi-bit adder
  - consider the logical operations affecting each signal
  - compute the output of each gate based on its input(s)
  - propagate outputs to inputs at every simulation time step

**ask** about anything you do not understand

- from any of the classes so far this semester (or the lecture notes)
- it will be too late for you to try to catch up later!
- I am always happy to explain things differently and practice examples with you

# glossary

**active-low** — a signal that is considered ‘true’ when 0.

**active-high** — a signal that is considered ‘true’ when 1.

**adder** — a logic circuit that implements 2’s complement addition between two words of data.

**bus** — a collection of signals all travelling between the same two points.

**carry** — a processor status bit indicating that the last arithmetic operation generated an unsigned overflow (a carry out of the MS bit).

**complement** — a bitwise logical operation that inverts every bit in a word.

**daisy chain** — connecting two or more devices or circuits in a linear fashion so that some output from one feeds into the input of the next.

**exclusive-or** — an ‘or’ operation that does not allow both inputs to be the same value.

**flag** — a single bit in the processor status register.

**full adder** — an adder that takes three single-bit inputs (two digits and a carry in) and produces two single-bit outputs (a sum and a carry out).

**functional block** — a high-level abstract component in a digital circuit that represents a reusable pattern of lower-level components or gates.

**gate** — an logic circuit component that implements a fundamental Boolean operation.

**half adder** — an adder that takes two single-digit inputs and produces a sum and carry output.

**multiplexer** — a digital circuit that connects one of  $2^n$  input signals to its output according to a  $n$ -bit select input.

**negative** — a processor status bit indicating that the result of the last arithmetic operation was negative, assuming the values involved were 2's complement integers.

**overflow** — a processor status bit indicating that the result of the last arithmetic operation generated a signed overflow (the result has the wrong sign), assuming the values involved were 2's complement integers.

**processor status register** — a register in the CPU holding several flags indicating whether the last arithmetic operation produced a zero or negative result, or whether an unsigned or signed overflow occurred.

**ripple-carry adder** — an adder constructed by daisy chaining several single-bit full adders together. The name arises because the sum and carry out at each bit position  $n$  cannot be computed until the carry out at position  $n - 1$  has been computed.

**select** — an input to a multiplexer that selects which of several other inputs should be connected to the output.

**signal** — anything that conveys a logic value from one place to another. In logic circuits, a signal is carried by a wire.

**subtractor** — a logic circuit that implements 2's complement subtraction between two words of data.

**wire** — a connection between several points in a circuit that forces them to all have the same logical value.

**zero** — a processor status bit indicating that the result of the last arithmetic operation generated a zero result (none of the result bits was 1).