

Computer Mathematics

Week 8 Examples

1. The *majority* function has three inputs. The output is true if two or more of the inputs are true.

(1) Draw the truth table for the *majority* function.

a	b	c	$\text{majority}(a, b, c)$
0	0	0	_____
0	0	1	_____
0	1	0	_____
0	1	1	_____
1	0	0	_____
1	0	1	_____
1	1	0	_____
1	1	1	_____


(2) Use a Karnaugh map to simplify the truth table of the *majority* function.

		ab			
		00	01	11	10
c	0	_____	_____	_____	_____
	1	_____	_____	_____	_____

(3) Draw the logic circuit that implements the *majority* function.

(4) What use can you think of for the *majority* function? What use can you think of for the *minority* function (whose output is true when the majority of input bits are zero)?

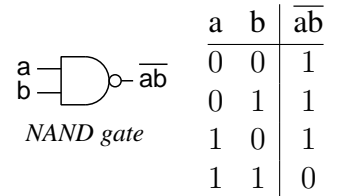2. Combining AND with NOT creates a NAND gate. NAND gates can be used to implement any logic function. (This is useful because some semiconductor technologies are most efficient when only one kind of gate is used.)



Using only NAND gates, draw logic circuits that implement the following basic Boolean operations:

NOT

AND

OR

3. Using only NAND gates, draw a logic circuit that implements XOR (exclusive OR).

4. Using only NAND gates, draw the logic circuit of a *half* adder: $\{ C, S \} = A + B$

5. Prove, using the simplest argument you can think of, that all of the examples above could also be implemented using only NOR gates.